

PRINT NAME (Last, First):

KEY

SIGN YOUR NAME:

STUDENT ID #:

CIRCLE ONE:

EE 100

EE 42

# 1	# 2	# 3	# 4	SUBTOTAL
6	14	10	12	42

# 5	# 6	# 7	SUBTOTAL	TOTAL
16	12	15	43	85

Instructions:

- 1 Print and sign your name and enter your student ID number above.
- 2 Read the questions carefully.
- 3 Write your solution clearly.
- 4 You must show your work to get full credit.
- 5 This exam has 7 questions worth 85 points, so you should proceed at approximately 1 point per minute.

Problem # 1 ($2 + 2 + 2 = 6$ points)

Let R, L, C denote resistance, inductance, and capacitance respectively.

What are the units of the following quantities in MKS units?

Express your answer in terms of meters, kilograms, seconds, and coulombs.

(a) L/R RL ckt time constant
 $\rightarrow L/R$ in seconds

Units of L/R are:

seconds

(b) RC RC ckt time constant
 \rightarrow seconds

Units of RC are:

seconds


(c) $LC = \frac{L}{R} \cdot RC \rightarrow$ seconds²

Units of LC are:



seconds²

Problem # 2 (2 + 2 + 2 + 8 = 14 points)

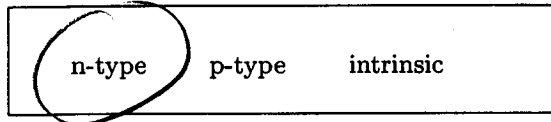- (a) If you dope pure silicon with a Group V element from the periodic table which kind of semiconductor do you get (circle the correct answer)?



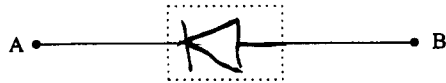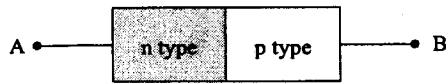- (b) Shown below is the cross-section of a pn-diode. In the dashed box, draw the circuit symbol of this diode.



- (c) Write a brief definition of a *hole* in a semiconductor and say why holes are significant.

A hole is an ambipolar positive charge carrier in a semiconductor - a missing electron, it permits us to make pn junctions, etc.

- (d) List 4 different solid-state diodes that are in common use and say briefly what each one does.

Rectifier - ordinary pn-diode conducts current in only one direction

Light-emitting diode - emits light when sufficiently forward biased

Laser diode - emits single-wavelength coherent light when sufficiently forward biased

Zener diode - has reverse-current conduction at a designable voltage

Solar cell - produces electric power in an electric load when illuminated

Varactor diode - acts as voltage-variable capacitance


Problem # 3 (5 + 5 = 10 points)

Shown below is a cross-sectional view of a silicon n-channel transistor.

There are various regions that you have to name (in the shaded boxes) and label (in the shaded circle).

- (a) Write the name of each region in the shaded box provided.
The names of these regions are the *source*, *drain*, *gate*, *bulk*, and *channel*.
- (b) In each shaded circle, enter the appropriate labels (1,2,3,4, III, V) that are defined below.
You may have to use several labels for some regions.


<u>label</u>	<u>meaning</u>
1	p-type region
2	n-type region
3	metal or heavily conducting region
4	insulator
III	regions containing dopants predominantly from Group III of the periodic table
V	regions containing dopants predominantly from Group V of the periodic table

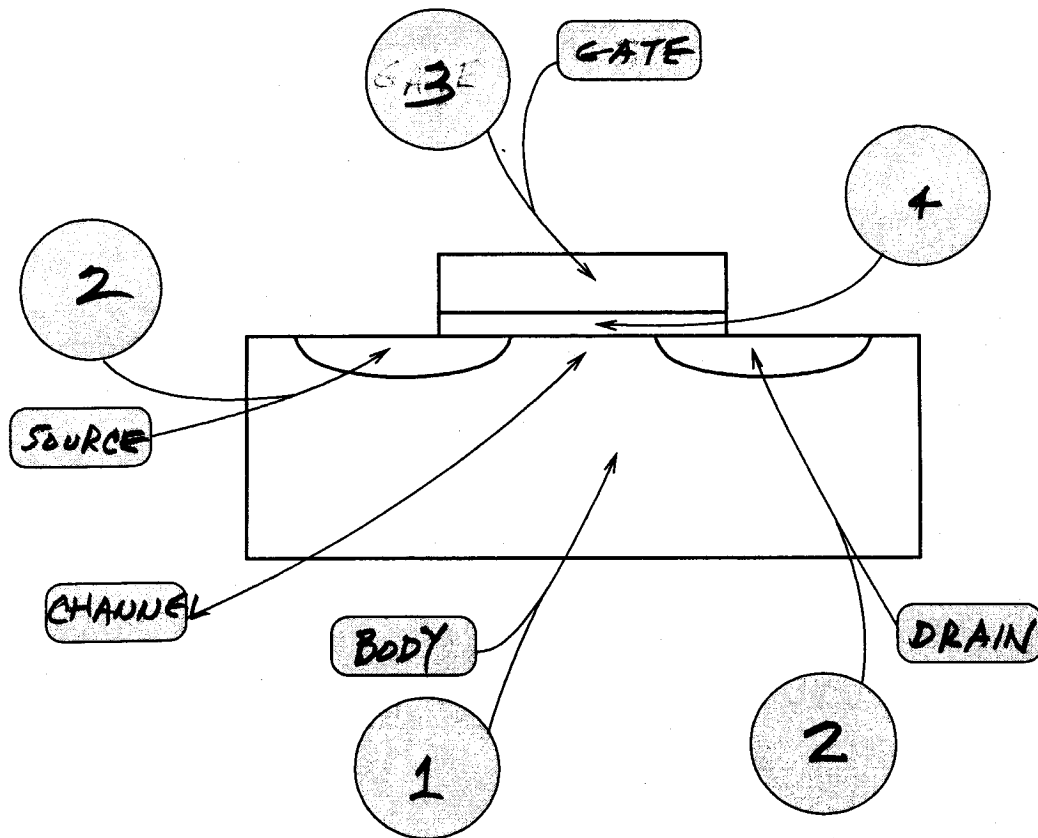

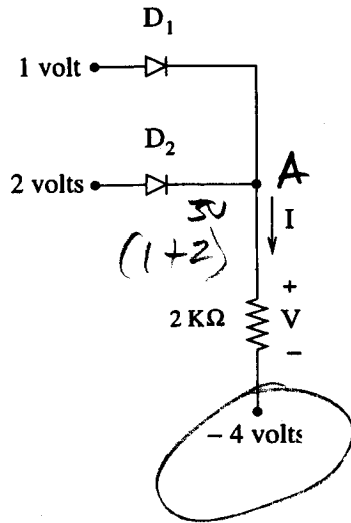Problem # 4 (4+4+2+2 = 12 points)

Consider the circuit shown below. The diodes are ideal.

For each diode, determine if it is conducting or not conducting.
Find I and V .



Assume D_2 conducting, D_1 off

$$\text{Then } I = \frac{2 - (-4)V}{R} = \frac{6V}{2K\Omega} = 3mA$$

$$V_A = -4 + (3mA)(2K\Omega) = +2V$$

> 1 VOLT so D_1 is not conducting

$$2V \rightarrow -4$$

Diode # 1 is conducting not conducting

(circle your choice)

Diode # 2 is conducting not conducting

(circle your choice)



$I = 3mA$

$V = +6V$

Problem # 5 (4 + 4 + 4 + 4 = 16 points)

Find the output resistance R_{out} for the circuit shown below.
We suggest the following steps:

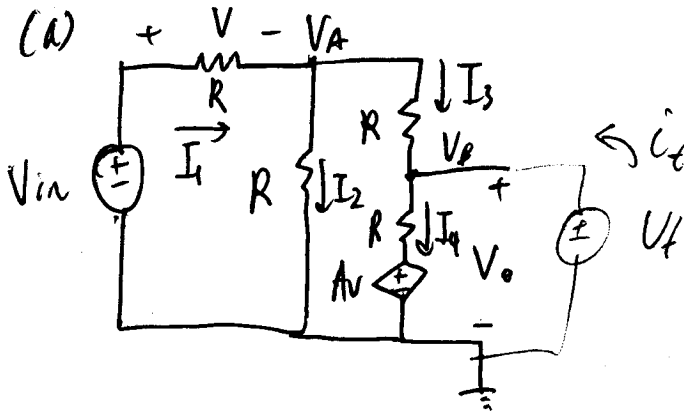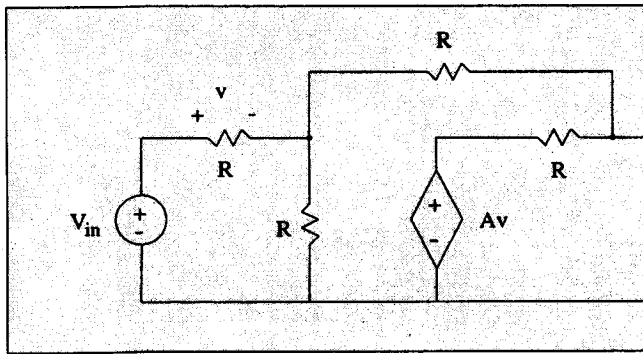- (a) Redraw the circuit you have to use to find the output resistance. (4 points)
- (b) Analyze this circuit. (8 points)
- (c) Show your algebra to find R_{out} . (4 points)



(b) $V_{in} \rightarrow 0$
Apply V_T , measure I_T
short V_{in}

$$I_1 = I_2 + I_3 \text{ @ } V_A$$

$$\textcircled{V_T} \Rightarrow I_T + I_3 = I_4$$

$$I_T = I_4 - I_3$$

$$I_4 = \frac{V_T - AV}{R} \quad \left\{ \begin{array}{l} V_A = 0 - V \Rightarrow V = -V_A \\ I_2 = \frac{V_A - V_T}{R} \end{array} \right.$$

$$I_2 = \frac{V_A - V_T}{R}$$

$$I_1 = \frac{0 - V_A}{R}$$

$$I_2 = \frac{V_A}{R}$$

$$I_1 = I_2 + I_3$$

$$-\frac{V_A}{R} = \frac{V_A}{R} + \frac{V_A - V_T}{R}$$

$$\frac{V_T}{R} = \frac{3V_A}{R}$$

$$V_T = 3V_A \Rightarrow V_A = \frac{V_T}{3}$$

$$I_T = I_4 - I_3$$

$$= \frac{V_T - A(-\frac{V_T}{3})}{R} - \frac{V_T/3 - V_T}{R}$$

$$\Rightarrow I_T(R) = V_T \left(1 + \frac{A}{3} - \frac{1}{3} + 1 \right)$$


$$= V_T \left(\frac{5}{3} + \frac{A}{3} \right) = V_T \left(\frac{5+A}{3} \right)$$

$$I_T = V_T \left(\frac{5+A}{3R} \right)$$

$$R_{out} = \frac{3R}{5+A}$$

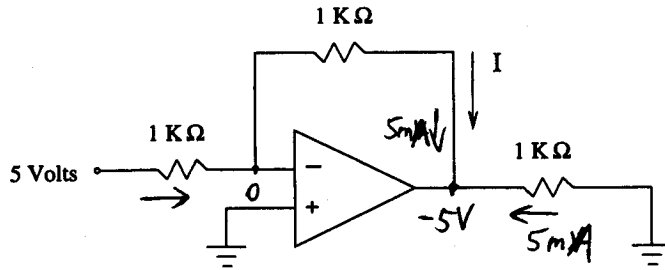Problem # 6 (4 + 4 + 4 = 12 points)

An ideal 5 volt DC source is connected to an inverting amplifier. The output of the amplifier is connected to a 1KΩ resistive load. The overall circuit is shown below. Assume that the op-amp behaves ideally.



(a) Find the current I .

$$\frac{5V - 0}{1K} = 5mA$$

$$I = 5mA$$

(b) How much power does the source deliver?

$$I_s = 5mA$$

$$V_s = 5V$$

$$P_s = I_s V_s = 25mW$$

$$\text{power delivered by source} = 25mW$$

(c) How much power does the op-amp deliver?

$$V_o = -5V$$

$$I_{op-amp} = -10mA$$



$$P_{op-amp} = -5V \cdot -10mA$$

$$= 50mW$$


$$\text{power delivered by op-amp} = 50mW$$

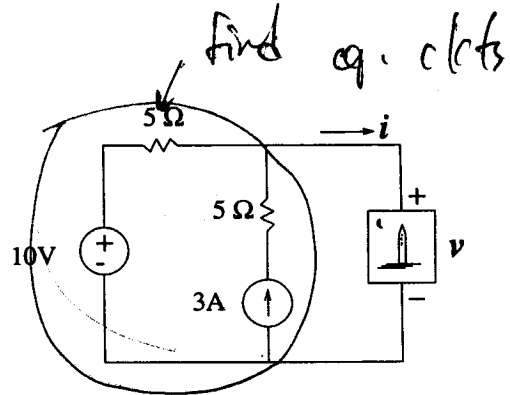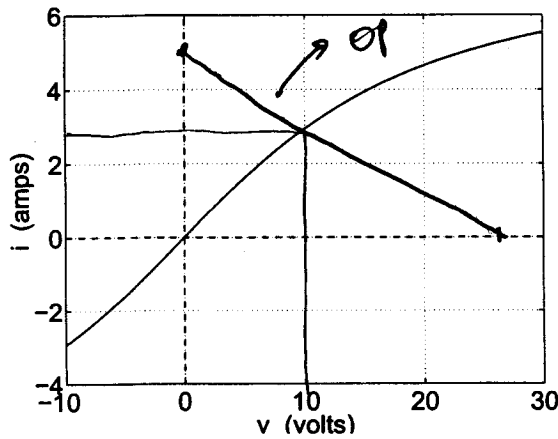Problem # 7 (4 + 4 + 1 + 2 + 2 + 2 = 15 points)


The resistive network shown below is connected to a berkelistor B. The berkelistor is a nonlinear device with $i - v$ characteristic shown below. Find the current i drawn by the berkelistor and the voltage v across the berkelistor.



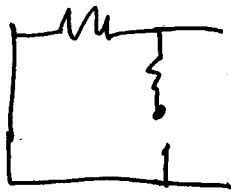
find $R_{th} \Rightarrow$ short all indep sources



$$R_{eq} = R_{th} = 5 \Omega$$

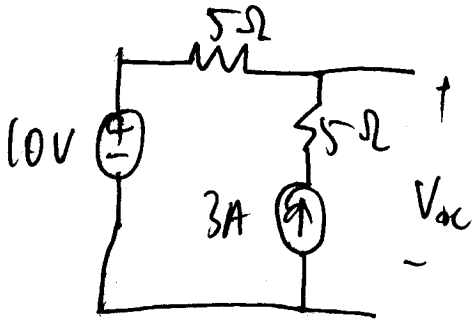
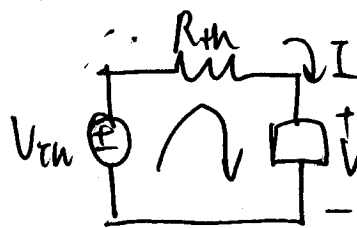
$$3A = \frac{V_{oc} - 10}{5} \Rightarrow V_{oc} = 25V$$



$$-V_{th} + I R_{th} + V = 0$$

$$V_{th} = I R_{th} + V$$

$$\textcircled{1} I = 0 \Rightarrow V = V_{th} = 25V$$

$$i = 3A$$

$$v = 10V$$

$$\textcircled{2} V = 0 \Rightarrow I = 5A$$